

2-5 型号为 SFS-40000/220 的三相三绕组变压器,容量比为 100/100/100,额定变比为 220/38.5/11,查得 $\Delta P_0 = 46.8 \text{ kW}$, $I_0 = 0.9\%$, $\Delta P_{S(1-2)} = 217 \text{ kW}$, $\Delta P_{S(1-3)} = 200.7 \text{ kW}$, $\Delta P_{S(2-3)} = 158.6 \text{ kW}$, $U_{S(1-2)} = 17\%$, $U_{S(1-3)} = 10.5\%$, $U_{S(2-3)} = 6\%$ 。试求归算到高压侧的变压器参数有名值。

$$\Delta P_{S1} = (\Delta P_{S(1-2)} + \Delta P_{S(1-3)} - \Delta P_{S(2-3)})/2 = 129.5 \text{ kW}$$

$$\Delta P_{S2} = (\Delta P_{S(1-2)} + \Delta P_{S(2-3)} - \Delta P_{S(1-3)})/2 = 87.45 \text{ kW}$$

$$\Delta P_{S3} = (\Delta P_{S(1-3)} + \Delta P_{S(2-3)} - \Delta P_{S(1-2)})/2 = 71.15 \text{ kW}$$

$$R_{T1} = \frac{\Delta P_{S1}}{S_N^2} U_N^2 = 3.919 \Omega \quad R_{T2} = \frac{\Delta P_{S2}}{S_N^2} U_N^2 = 2.645 \Omega \quad R_{T3} = \frac{\Delta P_{S3}}{S_N^2} U_N^2 = 2.152 \Omega$$

$$U_{S1}\% = (U_{S(1-2)}\% + U_{S(1-3)}\% - U_{S(2-3)}\%)/2 = 10.75$$

$$U_{S2}\% = (U_{S(1-2)}\% + U_{S(2-3)}\% - U_{S(1-3)}\%)/2 = 6.25$$

$$U_{S3}\% = (U_{S(1-3)}\% + U_{S(2-3)}\% - U_{S(1-2)}\%)/2 = -0.98$$

$$X_{T1} = \frac{U_{S1}\%}{100} \cdot \frac{U_N^2}{S_N} = 130.07 \Omega \quad X_{T2} = \frac{U_{S2}\%}{100} \cdot \frac{U_N^2}{S_N} = 75.65 \Omega \quad X_{T3} = \frac{U_{S3}\%}{100} \cdot \frac{U_N^2}{S_N} = -3.05 \Omega$$

$$G_T = \frac{\Delta P_0}{U_N^2} = 9.669 \times 10^{-7} \text{ S} \quad B_T = \frac{I_0\%}{100} \cdot \frac{S_N}{U_N^2} = 7.438 \times 10^{-6} \text{ S}$$

2-7 三台单相三绕组变压器组成三相变压器组,每台单相变压器的数据如下:额定容量为 30000 kV·A;容量比为 100/100/50;绕组额定电压为 127/69.86/38.5 kV; $\Delta P_0 = 19.67 \text{ kW}$; $I_0 = 0.332\%$; $\Delta P'_{S(1-2)} = 111 \text{ kW}$; $\Delta P'_{S(2-3)} = 92.33 \text{ kW}$; $\Delta P'_{S(1-3)} = 88.33 \text{ kW}$; $U_{S(1-2)} = 9.09\%$; $U_{S(2-3)} = 10.75\%$; $U_{S(1-3)} = 16.45\%$ 。试求三相接成 YN,yn,d 时变压器组的等值电路及归算到低压侧的参数有名值。

$$\text{额定电压为 } 127 / 69.86 / \frac{38.5}{\sqrt{3}} \text{ kV} = 127 / 69.86 / 22.28 \text{ kV}$$

$$\Delta P_{S(1-2)} = \left(\frac{S_N}{S_{N3}}\right)^2 \Delta P'_{S(1-2)} = 111 \text{ kW} \quad \Delta P_{S(1-3)} = \left(\frac{S_N}{S_{N3}}\right)^2 \Delta P'_{S(1-3)} = 353.32 \text{ kW}$$

$$\Delta P_{S(2-3)} = \left(\frac{S_N}{S_{N3}}\right)^2 \Delta P'_{S(2-3)} = 367.32 \text{ kW}$$

$$\Delta P_{S1} = (\Delta P_{S(1-2)} + \Delta P_{S(1-3)} - \Delta P_{S(2-3)})/2 = 47.5 \text{ kW}$$

$$\Delta P_{S2} = (\Delta P_{S(1-2)} + \Delta P_{S(2-3)} - \Delta P_{S(1-3)})/2 = 67.5 \text{ kW}$$

$$\Delta P_{S3} = (\Delta P_{S(1-3)} + \Delta P_{S(2-3)} - \Delta P_{S(1-2)})/2 = 30.82 \text{ kW}$$

$$R_{T1} = \frac{\Delta P_{S1}}{S_N^2} U_N^2 = 2.608 \times 10^{-2} \Omega \quad R_{T2} = \frac{\Delta P_{S2}}{S_N^2} U_N^2 = 3.486 \times 10^{-2} \Omega \quad R_{T3} = \frac{\Delta P_{S3}}{S_N^2} U_N^2 = 1.979 \times 10^{-2} \Omega$$

$$U_{S1} \dot{I}_0 = (U_{S(1-3)} \dot{I}_0 + U_{S(1-1)} \dot{I}_0 - U_{S(2-3)} \dot{I}_0) / 2 = 7.395$$

$$U_{S2} \dot{I}_0 = (U_{S(1-1)} \dot{I}_0 + U_{S(2-3)} \dot{I}_0 - U_{S(1-3)} \dot{I}_0) / 2 = 1.695$$

$$U_{S3} \dot{I}_0 = (U_{S(1-3)} \dot{I}_0 + U_{S(2-3)} \dot{I}_0 - U_{S(1-1)} \dot{I}_0) / 2 = 9.055$$

$$X_{T1} = \frac{U_{S1}^2}{100} \cdot \frac{U_N^2}{S_N} = 1.218 \Omega \quad X_{T2} = \frac{U_{S2}^2}{100} \cdot \frac{U_N^2}{S_N} = 0.279 \Omega \quad X_{T3} = \frac{U_{S3}^2}{100} \cdot \frac{U_N^2}{S_N} = 1.491 \Omega$$

$$G_T = \frac{\Delta P_0}{U_N^2} = 29.811 \times 10^{-6} S \quad B_T = \frac{I_N^2}{100} \cdot \frac{S_N}{U_N^2} = 2.015 \times 10^{-4} S$$

2-8 一台三相双绕组变压器, 已知: $S_N = 31500 \text{ kV} \cdot \text{A}$, $k_{TN} = 220/11$, $\Delta P_0 = 59 \text{ kW}$, $I_0 = 3.5\%$, $\Delta P_S = 208 \text{ kW}$, $U_S = 14\%$ 。

(1) 计算归算到高压侧的参数有名值;

(2) 作出 Π 型等值电路并计算其参数;


(3) 当高压侧运行电压为 210 kV, 变压器通过额定电流, 功率因数为 0.8 时, 忽略励磁电流, 计算 Π 型等值电路各支路的电流及低压侧的实际电压, 并说明不含磁耦合关系的 Π 型等值电路是怎样起到变压器作用的。

$$R_T = \frac{\Delta P_0}{\frac{S_N}{U_N^2} U_N^2} = 10.146 \Omega$$

$$X_T = \frac{U_N^2}{100} \cdot \frac{U_N^2}{S_N} = 215.111 \Omega$$

$$G_T = \frac{\Delta P_0}{U_N^2} = 1.219 S$$
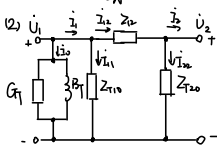
$$B_T = \frac{I_N^2}{100} \cdot \frac{S_N}{U_N^2} = 22.779 \times 10^{-6} S$$



$$k_T = \frac{U_{N1}}{U_{N2}} = \frac{220}{11} = 20 \quad Z_T = R_T + jX_T = (10.146 + j215.111) \Omega$$

$$Z_1 = \frac{Z_T}{k_T} = (0.507 + j10.756) \Omega$$

$$Z_{T10} = \frac{Z_T}{1-k_T} = (-0.534 - j11.322) \Omega \quad Z_{T20} = \frac{Z_T}{k_T(k_T-1)} = (0.027 + j0.566) \Omega$$

$$(3) \quad U_1 = \frac{210}{\sqrt{3}} \angle 0^\circ \text{ kV} = 121.244 \angle 0^\circ \text{ kV} \quad I_1 = I_N = \frac{S_N}{\sqrt{3} U_N} = 82.666 \text{ A}$$

$$\text{由于 } \lambda = \cos \varphi = 0.8, \quad \varphi = \arccos \lambda = 36.87^\circ, \quad \sin \varphi = 0.6.$$

$$I_{11} = I_1 \angle -\varphi = 82.666 \angle -36.87^\circ \text{ A}$$

$$\dot{I}_{11} = \frac{\dot{U}_1}{Z_{T10}} = 10.169 \times 10^3 \angle 92.7^\circ \text{ A} \quad \dot{I}_{12} = \dot{I}_1 - \dot{I}_{11} = 10749.85 \angle -86.96^\circ \text{ A}$$

$$\dot{U}_2 = \dot{U}_1 - \dot{I}_{12} Z_{12} = 5535.25 \angle -7.148^\circ \text{ V} \quad \text{低压侧电压 } U_{2L} = \sqrt{3} U_2 = 9.5874 \text{ kV}$$

$$\dot{I}_{22} = \frac{\dot{U}_2}{Z_{T20}} = 9767.5 \angle -94.448^\circ \text{ A} \quad \dot{I}_2 = \dot{I}_{12} - \dot{I}_{22} = 1660.05 \angle -36.896^\circ \text{ A}$$

由于 $Z_2 = Z_{T10} + Z_{12} + Z_{T20} = 0$, 构成谐振三角形, 将空载电流 I_0 分解成感性无功电流 I_{0L} 和容性无功电流 I_{0C} 。感性无功电流 I_{0L} 流过 Z_{12} 产生电压降 ΔU , 完成变压器两侧电压变换。