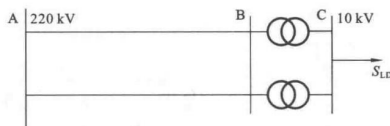
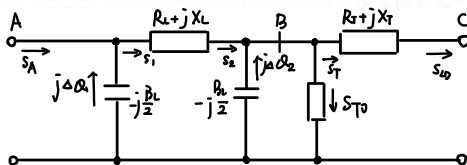


11-1 输电系统如题 11-1 图所示。已知：每台变压器 $S_N = 100 \text{ MV} \cdot \text{A}$, $\Delta P_0 = 450 \text{ kW}$, $\Delta Q_0 = 3500 \text{ kvar}$, $\Delta P_S = 1000 \text{ kW}$, $U_S = 12.5\%$, 工作在 -5% 的分接头；每回线路长 250 km , $r_1 = 0.08 \Omega/\text{km}$, $x_1 = 0.4 \Omega/\text{km}$, $b_1 = 2.8 \times 10^{-6} \text{ S/km}$; 负荷 $P_{LD} = 150 \text{ MW}$, $\cos\varphi = 0.85$ 。线路首端电压 $U_A = 245 \text{ kV}$, 试分别计算：



题 11-1 图

- (1) 输电线路、变压器以及输电系统的电压降落和电压损耗；
- (2) 输电线路首端功率和输电效率；
- (3) 线路首端 A、末端 B 及变压器低压侧 C 的电压偏移。



线路参数 $R_L = \frac{1}{2} r l = \frac{1}{2} \times 0.08 \times 250 = 10 \Omega$

$X_L = \frac{1}{2} x l = \frac{1}{2} \times 0.4 \times 250 = 50 \Omega$

$B_L = 2 b l = 2 \times 2.8 \times 10^{-6} \times 250 = 14 \times 10^{-5} \text{ S}$

变压器参数 $R_T = \frac{\Delta P_S U_N^2}{S_N^2} \times \frac{1}{2} = \frac{1000 \times 220^2}{100^2} \times \frac{1}{2} = 2.42 \Omega$

$X_T = \frac{U_{i0}^2}{100} \times \frac{U_N^2}{S_N} \times \frac{1}{2} = \frac{12.5}{100} \times \frac{220^2}{100} \times \frac{1}{2} = 30.25 \Omega$

$\Delta P_{T0} = 2 \Delta P_0 = 2 \times 450 \text{ kW} = 900 \text{ kW}$

$\Delta Q_{T0} = 2 \Delta Q_0 = 2 \times 3500 \text{ kvar} = 7000 \text{ kvar}$

$S_{T0} = \Delta P_{T0} + j \Delta Q_{T0} = (900 + j 7000) \text{ kVA} = (0.9 + j 7.0) \text{ MVA}$

假设各电压均为额定电压，计算功率分布

由 $P_{LD} = 150 \text{ MVA}$ $\cos\varphi = 0.85$ 则 $Q_{LD} = P_{LD} \tan\varphi = 92.9617 \text{ Mvar}$

$\Delta S_T = \frac{P_{LD}^2 + Q_{LD}^2}{U_N^2} (R_T + j X_T) = \frac{150^2 + 92.9617^2}{220^2} (2.42 + j 30.25) \text{ MVA}$

$= (1.55 + j 19.4637) \text{ MVA}$

$$S_T = S_{L1} + \Delta S_T = [(150 + j 92.9617) + (1.5571 + j 19.4637)] \text{ MVA}$$

$$= (151.5571 + j 112.4254) \text{ MVA}$$

$$\Delta Q_1 = \Delta Q_2 = \frac{P_L}{2} U_N^2 = 7 \times 10^{-4} \times 220^2 \text{ Mvar} = 33.88 \text{ Mvar}$$

$$S_2 = S_T + \Delta S_{T0} - j \Delta Q_2$$

$$= [(151.5571 + j 112.4254) + (0.9 + j 7.0) - j 33.88] \text{ MVA}$$

$$= (152.4571 + j 85.5454) \text{ MVA}$$

$$\Delta S_L = \frac{P_2^2 + Q_2^2}{U_N^2} (R_2^2 + j X_2^2) = \frac{152.4571^2 + 85.5454^2}{220^2} (10 + j 50) \text{ MVA}$$

$$= (6.3143 + j 31.5715) \text{ MVA}$$

$$S_1 = S_2 + \Delta S_L = [(152.4571 + j 85.5454) + (6.3143 + j 31.5715)] \text{ MVA}$$

$$= (158.7714 + j 117.1169) \text{ MVA}$$

$$S_A = S_1 - j \Delta Q_1 = [(158.7714 + j 117.1169) - j 33.88] \text{ MVA}$$

$$= (158.7714 + j 83.2369) \text{ MVA}$$

12. 输电线路:

电压降落:

$$\Delta U_L = \frac{P_L R_L + Q_L X_L}{U_A} + j \frac{P_L X_L - Q_L R_L}{U_A}$$

$$= \left(\frac{158.7714 \times 10 + 117.1169 \times 50}{245} + j \frac{158.7714 \times 50 - 117.1169 \times 10}{245} \right) \text{ kV}$$

$$= (30.3819 + j 27.6220) \text{ kV} = 41.0614 \angle 42.976^\circ \text{ kV}$$

$$U_B = \sqrt{(U_A - \Delta U)^2 + (\Delta U_{\perp})^2} = 216.3883 \text{ kV}$$

电压损耗: $U_A - U_B = (245 - 216.3883) \text{ kV} = 28.6117 \text{ kV}$

1b) 电压降落

电压降落

$$\begin{aligned} dU_T &= \frac{P_T R_T + Q_T X_T}{U_B} + j \frac{P_T X_T - Q_T R_T}{U_B} \\ &= \left(\frac{151.5571 \times 2.42 + 112.9259 \times 30.75}{216.3883} + j \frac{151.5571 \times 30.75 - 112.9259 \times 2.42}{216.3883} \right) \text{KV} \\ &= (17.9115 + j 19.7296) \text{KV} = 26.4641 \angle 48.859^\circ \text{KV} \end{aligned}$$

$$U_C = \sqrt{(U_B - dU_T)^2 + (dU_T)^2} = 199.9724 \text{KV}$$

电压损耗 $U_B - U_C = (216.3883 - 199.9724) \text{KV} = 16.4159 \text{KV}$

1c) 输电系统

电压降落 $dU = dU_C + dU_T = [(30.3819 + j 27.6220) + (17.9115 + j 19.7296)] \text{KV}$
 $= (47.7934 + j 47.5516) \text{KV}$

电压损耗 $U_A - U_C = (245 - 199.9724) \text{KV} = 45.0276 \text{KV}$

12) 首端功率 $S_4 = (158.7714 + j 83.2369) \text{MVA}$

输电效率 $\eta = \frac{P_{LD}}{P_A} \times 100\% = \frac{150}{158.7714} \times 100\% = 94.48\%$

13) 点A电压偏移 $\frac{U_A - U_N}{U_N} \times 100\% = \frac{245 - 220}{220} \times 100\% = 11.36\%$

点B电压偏移 $\frac{U_B - U_N}{U_N} \times 100\% = \frac{216.3883 - 220}{220} \times 100\% = -1.64\%$

变压器实际变比 $k_T = \frac{220(1 - 0.05)}{11} = \frac{209}{11} = 19$

点C实际电压 $U_C = \frac{U_C'}{k_T} = \frac{199.9724}{19} \text{KV} = 10.5248 \text{KV}$

点C电压偏移 $\frac{U_C - U_N}{U_N} \times 100\% = \frac{10.5248 - 10}{10} \times 100\% = 5.25\%$