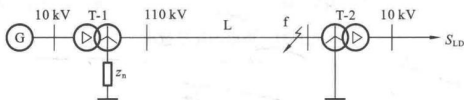


7-3 系统接线如题 7-3 图所示, 已知各元件参数如下。发电机 G: $S_N = 30 \text{ MV} \cdot \text{A}$, $x_d'' = x_{(2)} = 0.2$; 变压器 T-1: $S_N = 30 \text{ MV} \cdot \text{A}$, $U_S = 10.5\%$, 中性点接地阻抗 $z_n = j10 \Omega$; 线路 L: $l = 60 \text{ km}$, $x_{(1)} = 0.4 \Omega/\text{km}$, $x_{(0)} = 3x_{(1)}$; 变压器 T-2: $S_N = 30 \text{ MV} \cdot \text{A}$, $U_S = 10.5\%$; 负荷: $S_{LD} = 25 \text{ MV} \cdot \text{A}$ 。试计算各元件电抗的标么值, 并作出各序网络。



题 7-3 图

选取 $S_B = 30 \text{ MVA}$, $U_B = U_{av}$

$$X_{d(2)} = X_d'' = 0.2 \frac{S_B}{S_{Gm}} = 0.2 \times \frac{30}{30} = 0.2$$

$$X_{T1} = \frac{U_{S1}\%}{100} \frac{S_B}{S_{TN}} = \frac{10.5}{100} \times \frac{30}{30} = 0.105$$


$$X_{L(1)} = X_{L(2)} = X_{L(0)} l \frac{S_B}{U_B^2} = 0.4 \times 60 \times \frac{30}{115^2} = 0.0544$$

$$X_{L(0)} = 3X_{L(1)} = 3 \times 0.0544 = 0.1632$$


$$X_{LD(1)} = 1.2 \frac{S_B}{S_{LD}} = 1.2 \times \frac{30}{25} = 1.44 \quad X_{LD(2)} = 0.35 \frac{S_B}{S_{LD}} = 0.35 \times \frac{30}{25} = 0.42$$

$$Z_n = j10 \frac{S_B}{U_B^2} = j0.0227 \quad 3Z_n = ja0.06805$$

正序网络

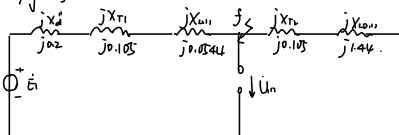

负序网络

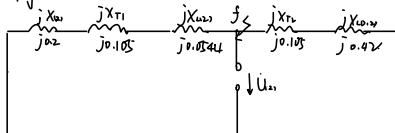

零序网络

